

Lab Assignment #5

Instructor: Dr. Ioannis Savidis

TA: Ying Teng E-Mail: yt74@drexel.edu

Drexel University**Electrical and Computer Engineering****Oct 23rd, 2013 (Wednesday, week 5)**

1 Objective

The goal of this assignment is learn how to build a CMOS gate using transistors. The major goals are to learn:

- The basic principles of designing the *Nand* and the *And* gates;
- The characteristics of *Nand* and the *And* CMOS gates.

2 Assignments

The objective of this laboratory is to design and simulate the **Nand** and the **And** gate.

2.1 Design an Nand Gate

1. Design a two input **Nand** gate, where the inputs are labeled **a** and **b**, and the output is labeled **out**. Make sure the total cell height is 35um for standard cell design. Choose **Vdd** and **Gnd** with width of 5um. Draw the Schematic and Layout of **Nand** Gate as shown in Figure 1 and Figure 2, respectively.
2. Check design using DRC.
3. Verify your design using LVS.
4. Simulate Schematic and Layout.

2.2 Design an And Gate

1. Design an **And** gate in schematic view as shown in Figure 3.
2. In layout view, connect the designed **Nand** and **Inverter** to form an **And** gate in a logic row as shown in Figure 4.
3. Perform DRC and LVS check.
4. Simulate the **And** gate.

 


Figure 1: A schematic illustration of the *Nand* gate.

2.3 Deliverables

Lab 5 is due by Friday Nov. 1st at 5 pm. Your report should include the following:

- The schematic view and the layout view of both the **Nand** gate and the **And** gate. Use rulers to measure the dimension of the **Nand** gate and the **And** gate in layout views.
- Show DRC and LVS results for both the **Nand** gate and the **And** gate.
- Perform transient simulations on both the schematic views and the layout views of the **Nand** gate and the **And** gate to check the functionality, respectively.
- Measure the worst-case propagation delay, rise and fall time for an ideal pulse input (Use markers in the waveform analyzer to demarcate the various timing properties) for both **Nand** and **And** gates based on the simulation results.
- Perform a DC simulation on the schematic view of the **Nand** gate to plot the V_{in} versus V_{out} curve. Use markers to show the switching threshold. Size the PMOS to make the **Nand** symmetrical.

- Since both the designed **Inverter** and **Nand** are symmetrical, perform a DC simulation on the **And** gate to observe if it is also a symmetrical gate (Use markers to show the result).

 


Figure 2: A layout illustration of the *Nand* gate.

 


Figure 3: A schematic illustration of the *And* gate.

 


Figure 4: A layout illustration of the *And* gate.