



Drexel University  
Electrical and Computer Engineering Department

**ECEC 471**  
**Introduction to VLSI Design**

Lab Assignments 2,3,4  
October 23rd, 2013

Julian Kemmerer  
jvk@drexel.edu

## Lab 2 + 3

Labs 2 and 3 complete schematic and layout based simulations to characterize inverter function. Lab 3 specifically sizes the PMOS transistor channel width such that the switching threshold is half of  $V_{dd}$ .

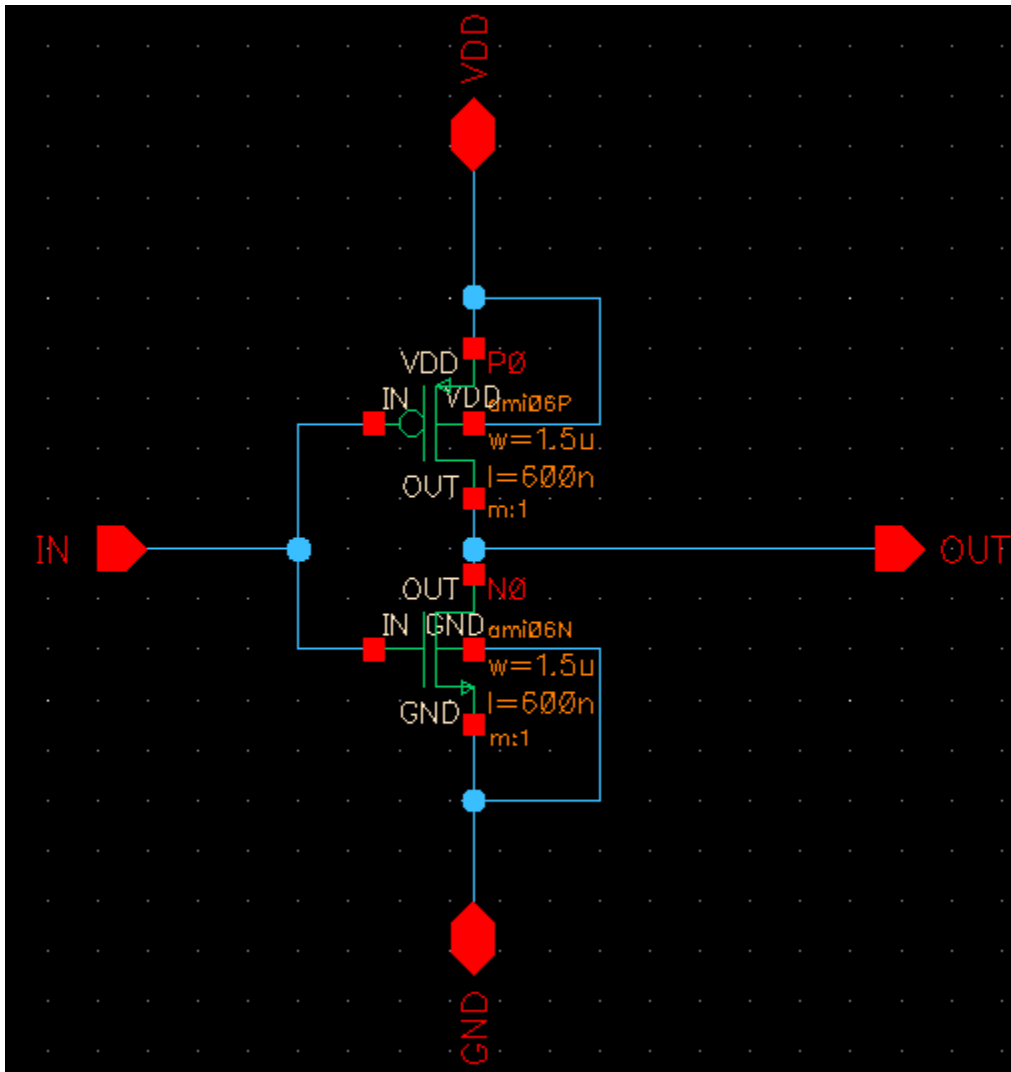


Figure 1. Schematic view of the inverter

 


Figure 2. Layout view of the inverter

 


Figure 3. Extracted view of the inverter

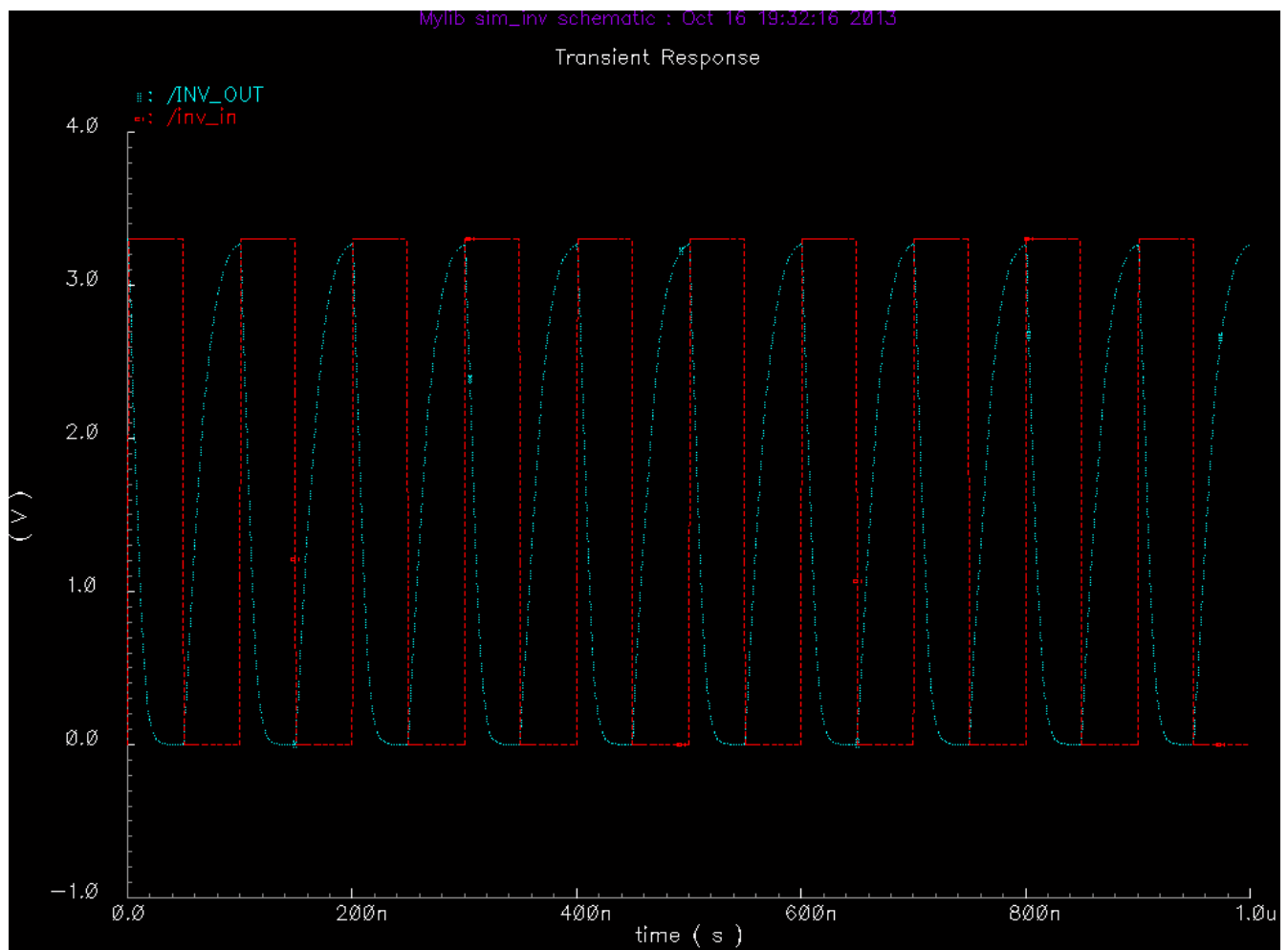


Figure 4. Schematic-based transient simulation

Note: Propagation delay, DRC, LVS, and layout based simulations were only collected during Lab 3 (after the switching threshold PMOS sizing, i.e. No layout based data was collected during Lab 2, only during Lab 3)

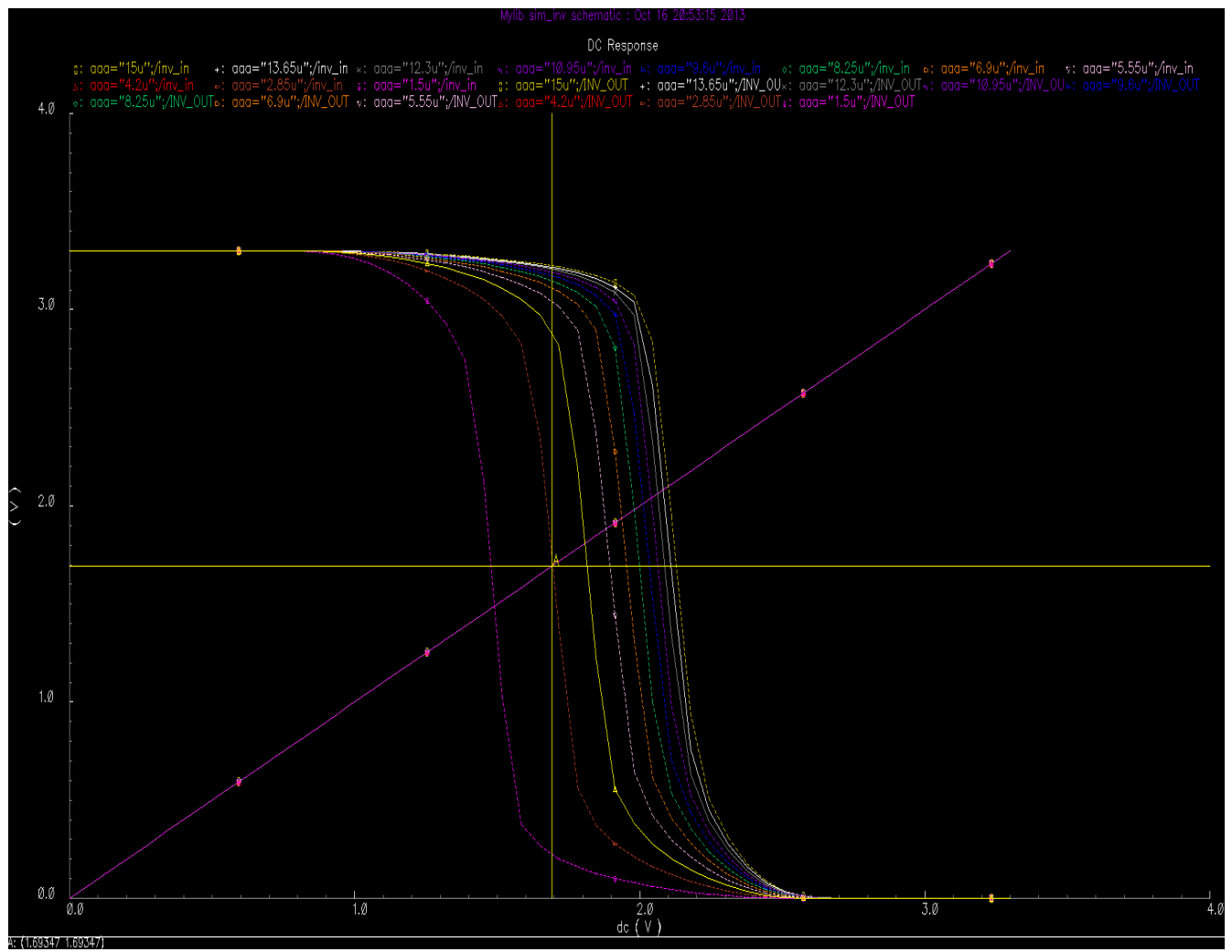


Figure 5. DC sweep simulation plot used to choose the channel width

PMOS Width: 2.85 um  
NMOS Width: 1.5 um

 


Figure 6. Layout view of the symmetrical inverter

 


Figure 7. Extracted view of the symmetrical inverter



```

DRC started.....Wed Oct 16 23:39:31 2013
completed ....Wed Oct 16 23:39:31 2013
CPU TIME = 00:00:00  TOTAL TIME = 00:00:00
***** Summary of rule violations for cell "std_inv_15 layout" *****
Total errors found: 0

```

Figure 8. DRC verification results for symmetrical inverter

```

LVS job is now started...
The LVS job has completed. The net-lists match.
Run Directory: /home/DREXEL/jvk27/ECE471/LVS

```

Figure 9. LVS verification results symmetrical inverter

 


Figure 10. DC simulation results for schematic view (no extracted caps)

 


Figure 11. DC simulation results for layout view (included extracted caps)

 


Figure 12. Transient simulation result for the newly designed symmetrical inverter

 


Figure 13. Transient simulation result for the newly designed symmetrical inverter with critical points marked (see below).

Table 1. Marker values and units

Marker	Value	Unit
M1	1.65	V
M2	300.499	ns
M3	308.174	ns
M4	349.497	ns
M5	355.536	ns

The critical points (M2 through 5) marked above are the  $\frac{1}{2} V_{dd}$  (M1) time points for rising and falling propagation. Thus the rise and fall propagation times can be calculated as:

$$\text{Rising input propagation} = M3 - M2 = 7.675 \text{ ns}$$

$$\text{Falling input propagation} = M5 - M4 = 6.039 \text{ ns}$$

## Lab 4

This lab evaluates the sizing of inverters in a chain and examines the operating frequency of a 21-inverter ring oscillator. The chain of inverters is first optimized to minimize the propagation delay from input to output when driving a load capacitance. Next, all inverters in the chain are made equal-sized and the propagation delay is examined once more as the inverter sizes are swept over a range.

The optimal number of inverters in a chain is given in the equation below (1).

$$f = \sqrt[n]{C_l/C_{gin}} \quad (1)$$

Where  $f$  is the sizing factor,  $n$  is the number of stages,  $C_l$  is the load capacitance, and  $C_{gin}$  is the first gate input capacitance. (1) can be solved for  $n$ .

$$n = \ln \frac{C_l}{C_{gin}} \quad (2)$$

$$\begin{aligned} C_l &= 1 \text{ pF} \\ C_{gin} &= 10 \text{ fF} \\ f &= e \\ n &= 4.6 \approx 4 \end{aligned} \quad (3)$$

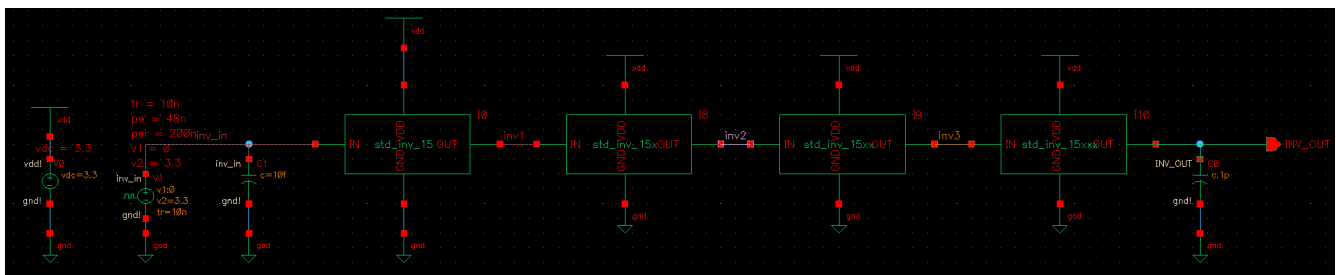


Figure 14. Schematic view of the inverter chain

 


Figure 15. Simulation waveform

 


Figure 16. Simulation waveform (zoomed) with markers delineating the rising propagation delay of 2.1 ns

 


Figure 17. Simulation waveform (zoomed) with markers delineating the falling propagation delay of 1.8 ns

Using simulations results, the rise/fall (labeled as *transitions* below) propagation for each inverter was measured.

Table 2. Transition times for each inverter in the chain

	Transition 1	Transition 2	Average Transition
Inverter	Time (ns)	Time (ns)	Time (ns)
INV1	1.1392	0.8398	0.9895
INV2	0.4148	0.3384	0.3766
INV3	0.2096	0.2519	0.23075
INV4	0.3681	0.344	0.35605

The total propagation delay (as measured from the input to the first inverter to the output of the last) is shown below.

Table 3. Propagation delay through the entire chain

Transition 1	Transition 2	Average Transition
Time (ns)	Time (ns)	Time (ns)
2.1279	1.7812	1.95455

Note: The sum of the average transition times for each inverter (Table 2) equals the value shown for the average total propagation delay through the entire chain (Table 3).



Compared to the same capacitive load being driven by a single inverter (Table 1, avg=6.857 ns) the chain is able to drive the load roughly ~3.5 times faster.

 


Figure 18. Sweep of inverter size from NMOS width=1.5 um 5.0 um and resulting transient waveforms  
Note: The ratio of PMOS to NMOS as computed in Lab 3 was 1.9. Thus, to maintain this ratio, the PMOS width was swept from 2.85 um to 9.5 um during this process.

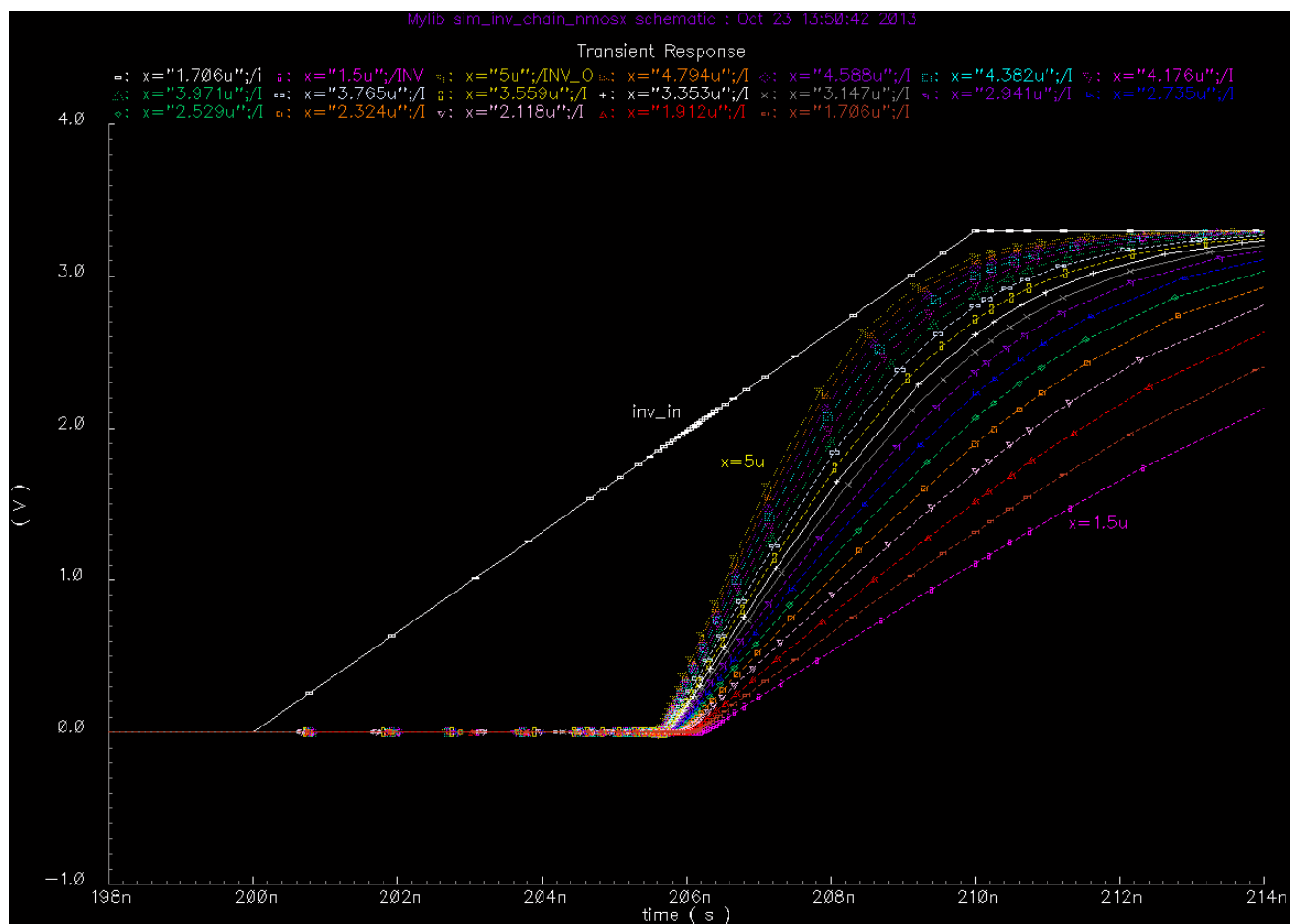


Figure 19. Rising portion of the resulting transient waveforms for sweep of inverter size

 


Table 3. Rise and fall times as a function of transistor width

NMOS Width (um)	Rise Time (ns)	Fall Time (ns)
5	2.16	2.65
4.794	2.25	2.73
4.588	2.34	2.81
4.382	2.44	2.9
4.176	2.54	2.99
3.971	2.67	3.1
3.765	2.79	3.25
3.559	2.93	3.39
3.353	3.08	3.54
3.147	3.28	3.73
2.941	3.51	3.97
2.735	3.74	4.23
2.529	4.05	4.56
2.324	4.4	4.96
2.118	4.84	5.48
1.912	5.37	6.15
1.706	6.05	7.06
1.5	6.95	8.34

Propagation Delay as Function of Invertor Size

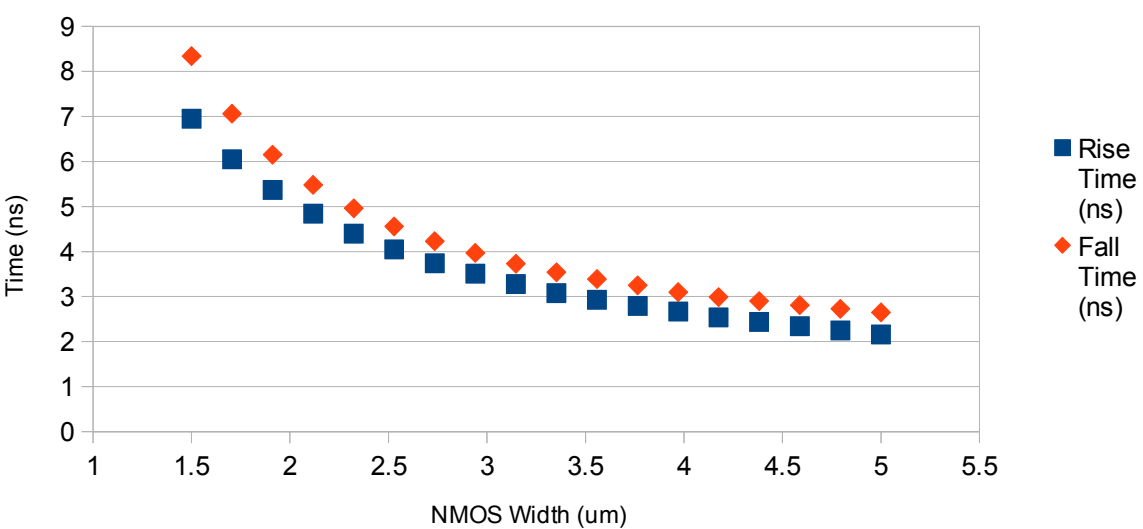


Figure 21. Change in propagation delay as a function of the size of the inverters

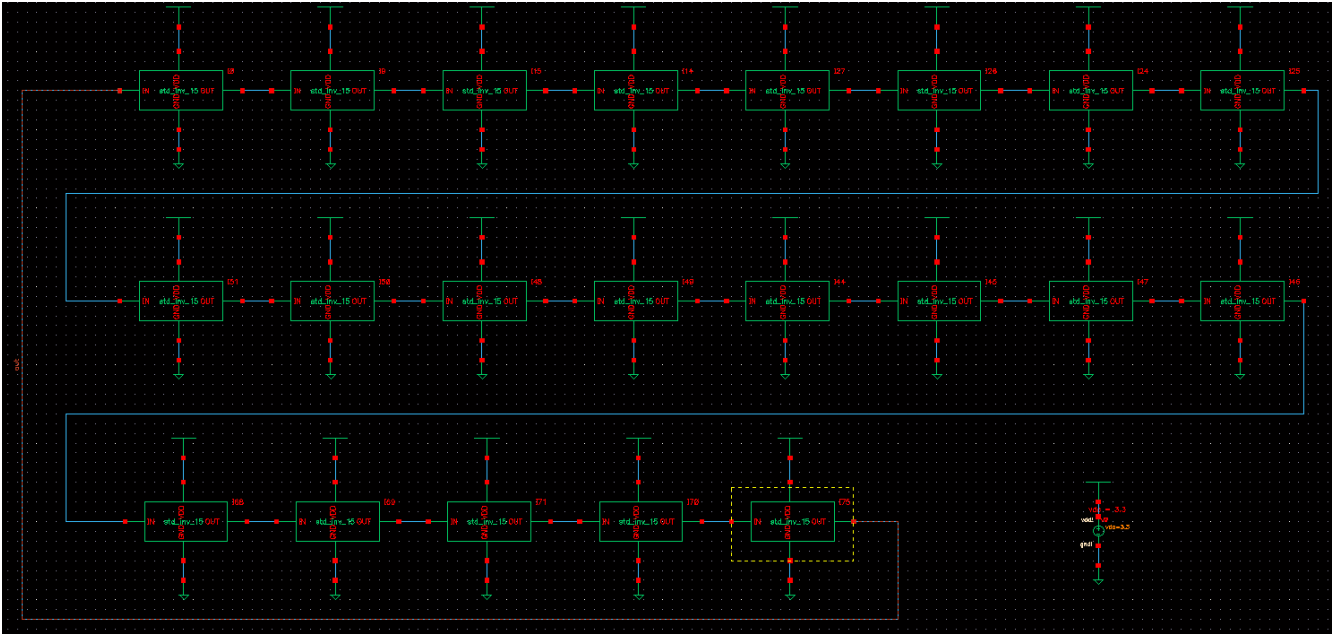


Figure 22. Schematic view of ring oscillator

 


Figure 22. Waveform generated by the ring oscillator showing period = 9.5 ns, freq = 105.4 MHz